

Project 3. MIPS Multicycle Microarchitecture

Pre-silicon Verification - Spring 2022



TEAM:

LUIS ANGEL BUSTAMANTE ROSAS
ABRAHAM JOSUE DELGADO NAVA
OSVALDO DAMIAN CRUZ LOPEZ
RICARDO BAZALDÚA CALDERÓN

June 19rd, 2022

MIPS ARCHITECTURE

CONTENTS

SUMMARY	2
INTRODUCTION	3
DESIGN DESCRIPTION	4
HDL IMPLEMENTATION	6
Top level Design	6
Test Bench	11
CONTROL UNIT	12
CONTROL FSM	13
ALU	25
ALU CONTROL	25
DATA MEMORY	26
INSTRUCTIONS MEMORY	27
FILE REGISTER	28
SIGN EXTENDER	29
MULTIPLEXER	29
BRANCH DECODER	30
LATCH	31
DETAILED DESCRIPTION OF VERIFICATION PROCESS	32
TEST PROGRAM	32
OBJECTIVE	32
DESIRED RESULTS	32
PROGRAM FLOWCHART	33
C CODE	34
ASSEMBLER AND MACHINE CODE	35
RESULTS	36
EDA Playground PROJECT LINK	36
CONCLUSIONS	37
FUTURE WORK	37
REFERENCES	37

SUMMARY

This document will discuss the development of the MIPS Multicycle Microarchitecture, which has been designed with the necessary modules to follow multiple data paths according to the type of instruction (R,I or J) and execute a large number of instruction just like the Monocycle architecture but dividing the execution of each instruction in several smaller cycles.

This architecture allows each instruction to use the number of cycles it needs.

In the introduction we will discuss a little about the mips architecture and the differences between the monocycle and multicycle architecture.

Later, in the description of the design, the block diagram of the multicycle architecture will be described, highlighting the differences and advantages it has with the previous design (the unicycle architecture) as well as the new blocks implemented in this design.

Consequently, the HDL implementation used in the design is presented, as well as the description of the process and test program.

After that , the flowchart of the simulated program, its assembler and machine code, the results obtained in the simulations and their description are presented.

Finally, the conclusions will be made with the knowledge acquired and the possible future works that this project generated will be proposed.

INTRODUCTION

MIPS (Microprocessor without Interlocked Pipe Stages) is a general purpose processor architecture designed to be implemented on a single VLSI chip. The main goal of the design is high performance in the execution of compiled code. The architecture is experimental since it is a radical break with the trend of modern computer architectures. The basic philosophy of MIPS is to present an instruction set that is a compiler-driven encoding of the microengine.


MIPS is designed for high performance. To allow the user to get maximum performance, the complexity of individual instructions is minimized. This allows the execution of these instructions at significantly higher speeds. To take advantage of simpler hardware and an instruction set that easily maps to the microinstruction set, additional compiler-type translation is needed. This compiler technology makes a compact and time-efficient mapping between higher level constructs and the simplified instruction set.

If data operands are used repeatedly in a basic block of code, having them in registers will prevent redundant load/stores and redundant addressing calculations; this allows higher throughput since more operations directly related to the computation can be performed.

A unicycle datapath is characterized in that the execution of each instruction lasts for one clock cycle. Since the clock cycle must be adapted to the needs of the execution of all instructions and needs to adjust its duration to that of whichever instruction is longer. But the time required for execution can vary appreciably from one instruction to another. So a jump or jump unconditionally takes much less time than, say, a load.


In the first place, one might think that a monocycle processor is faster than a multicycle one since the first would only require, as its name indicates, a single cycle to carry out any instruction, while the second would require more than one. The problem is that the monocycle processor actually requires as much time to execute any instruction as it does to execute the most complex instruction. On the other hand, since all possible operations need to be implemented in a single cycle, it is necessary to have the ability to do calculations at various times. and, therefore, several ALUs are required. The multicycle implementation gets rid of these problems and, by requiring less hardware, it would also imply a reduction in power consumption.

DESIGN DESCRIPTION

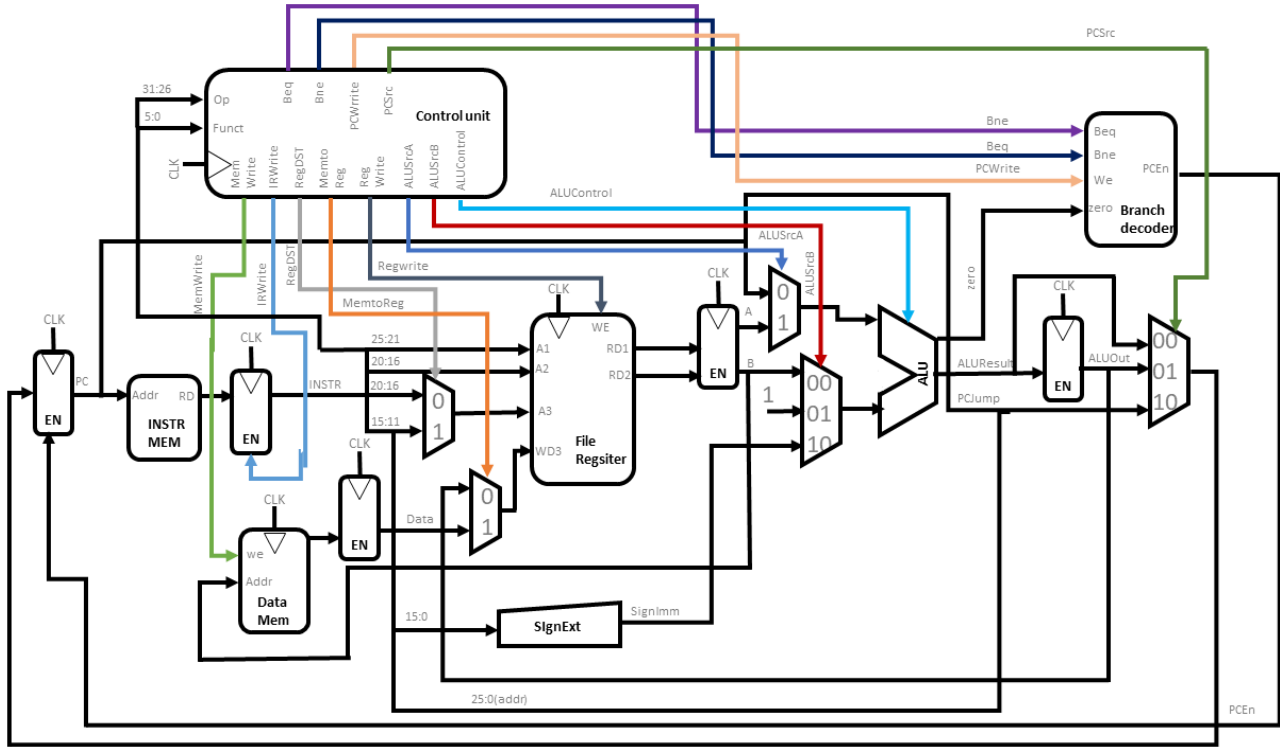


In this design we take the monocycle design previously designed and eliminate the extra modules we will not use in this architecture, also the control unit was modified, using a state machine, and some registers were added in the end of some process to be able to save the data at the end of the shorter cycles.

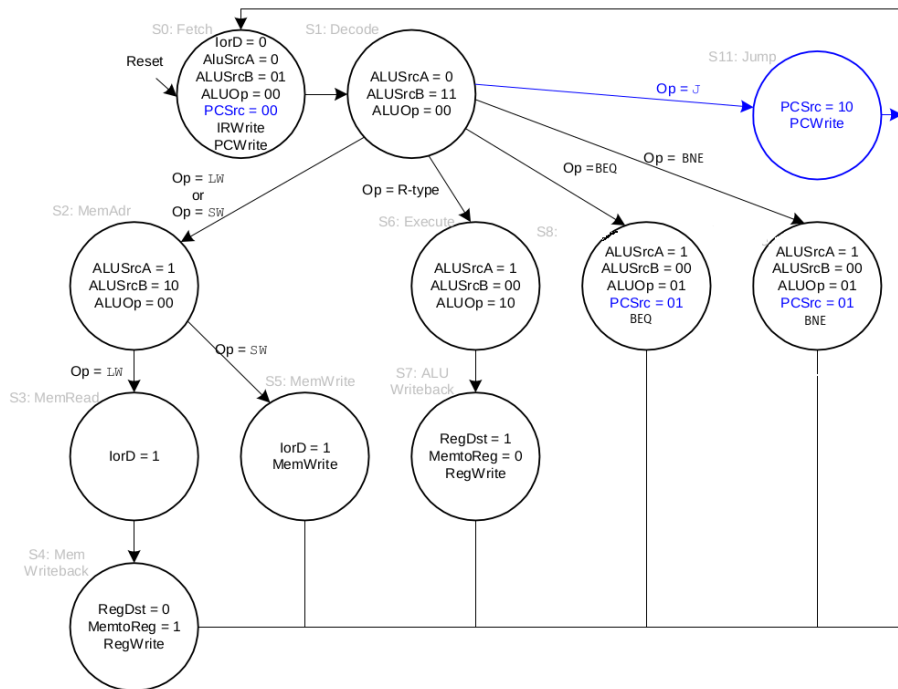Due to the nature of the control unit, for its elaboration an FSM (finite state machine) diagram was used, which contains the sequence followed by this state machine and is presented below.



In this diagram we can observe the path followed by the processor in each instruction and it is more notable how some instructions run faster than others.

Although the unicycle approach is easy to understand, it is not practical since all instructions take the same time (one cycle) to complete; the clock cycle will have to adapt to the slowest. A realization would be better than allowing different instructions to take a different number of cycles, the size of the much shorter cycle. Thus, the instructions can be divided into different steps according to the unit's functions that will be used during the execution of the different stages. These allow circuitry to be shared allowing one functional unit to be used on more than one occasion during the execution of the same instruction, as long as it is done for different cycles.

 

This division of instructions is possible thanks to the registers added in the design, these were added as new modules in the design and allow saving the data of the instruction between cycles. Two different types of registers were added, one with the writing always enabled and the other one with the writing controlled by a variable.

HDL IMPLEMENTATION

Top level Design

```
`include "latch.v"
`include "ALU.v"
`include "control_unit.v"
`include "data_memory.v"
`include "inst_mem.v"
`include "register_file.v"
`include "SignExt.v"
`include "mux2to1.v"
`include "mux3to1.v"
`include "branch_decoder.v"

module MIPS_multicycle (input clk, rst);
  /*-----Define internal nets-----*/
  wire      [31:0]  PC_w, PCNext_w, Inst_w, InstLatched_w,
                Reg1_w, Reg1Latched_w, Reg2_w, Reg2Latched_w,
                SignE_w, SrcA_w, SrcB_w, ALUResult_w, ALUOut_w,
                DataM_w, DataMLatched_w, RegWD_w;

  wire      [4:0]   RegWA_w;
  wire      [3:0]   ALU_Ctl_w;
  wire      [1:0]   ALUSrcB_w, PCSrc_w;

  wire           MemtoReg_w, RegDst_w, ALUSrcA_w,
                IRWrite_w, MemWrite_w, PCWrite_w, BEQ_w, BNE_w,
                RegWrite_w, PCEn_w, zero_w;

  /*-----Module instantiations-----*/
  //////////// INSTRUCTIONS MEMORY ////////////
  inst_mem MIPS_inst_mem (
    .address(PC_w),
    .inst(Inst_w)
  );

  //////////// FILE REGISTER ////////////
  register_file MIPS_register_file (
```

```

        .clk(clk),
        .regWrite(RegWrite_w),
        .readReg1(InstLatched_w[25:21]),
        .readReg2(InstLatched_w[20:16]),
        .writeReg(RegWA_w),
        .writeData(RegWD_w),
        .readData1(Reg1_w),
        .readData2(Reg2_w)
    );

    //////////// ALU OPERATIONS ////////////
    ALU MIPS_ALU (
        .ALU_Ctl(ALU_Ctl_w),
        .A(SrcA_w),
        .B(SrcB_w),
        .ALUOut(ALUResult_w),
        .Zero(zero_w)
    );

    //////////// DATA MEMORY ////////////
    data_memory MIPS_data_memory (
        .clk(clk),
        .address(ALUOut_w),
        .memWrite(MemWrite_w),
        .writeData(Reg2Latched_w),
        .readData(DataM_w)
    );

    //////////// SIGN EXTENDER ////////////
    SignExt MIPS_SignExt (
        .data_in(InstLatched_w[15:0]),
        .data_out(SignE_w)
    );

    //////////// BRANCH DECODER ////////////
    branch_decoder MIPS_branch_decoder (
        .beq(BEQ_w),
        .bne(BNE_w),
        .pcwrite(PCWrite_w),
        .zero(zero_w),
        .ctrl(PCEn_w)
    );

```



```

);

////////// CONTROL UNIT //////////

control_unit MIPS_control_unit (
    .clk(clk),
    .rst(rst),
    .Opcode(InstLatched_w[31:26]),
    .Funct(InstLatched_w[5:0]),
    .MemtoReg(MemtoReg_w),
    .RegDst(RegDst_w),
    .ALUSrcA(ALUSrcA_w),
    .ALUSrcB(ALUSrcB_w),
    .PCSrc(PCSrc_w),
    .IRWrite(IRWrite_w),
    .MemWrite(MemWrite_w),
    .PCWrite(PCWrite_w),
    .BEQ(BEQ_w),
    .BNE(BNE_w),
    .RegWrite(RegWrite_w),
    .ALU_Ctl(ALU_Ctl_w)
);

/*-----Multiplexers-----*/

////////// MUX RegDst //////////
mux2to1 #(.WORD_LENGTH(5)) MIPS_mux_RegDst (
    .sel(RegDst_w),
    .Data_0(InstLatched_w[20:16]),
    .Data_1(InstLatched_w[15:11]),
    .Mux_Output(RegWA_w)
);

////////// MUX MemtoReg //////////
mux2to1 MIPS_mux_MemtoReg (
    .sel(MemtoReg_w),
    .Data_0(ALUOut_w),
    .Data_1(DataMLatched_w),
    .Mux_Output(RegWD_w)
);

```

```

////////// MUX ALUSrcA //////////
mux2to1 MIPS_mux_ALUSrcA(
    .sel(ALUSrcA_w),
    .Data_0(PC_w),
    .Data_1(Reg1Latched_w),
    .Mux_Output(SrcA_w)
);

////////// MUX ALUSrcB //////////
mux3to1 MIPS_mux_ALUSrcB(
    .sel(ALUSrcB_w),
    .Data_0(Reg2Latched_w),
    .Data_1(32'd1),
    .Data_2(SignE_w),
    .Mux_Output(SrcB_w)
);

////////// MUX PCSrc //////////
mux3to1 MIPS_mux_PCSrc(
    .sel(PCSrc_w),
    .Data_0(ALUResult_w),
    .Data_1(ALUOut_w),
    .Data_2({PC_w[31:26], InstLatched_w[25:0]}),
    .Mux_Output(PCNext_w)
);

/*-----Latches-----*/
////////// LATCH PC //////////
latch MIPS_latch_PC(
    .clk(clk),
    .rst(rst),
    .en(PCEn_w),
    .in(PCNext_w),
    .out(PC_w)
);

////////// LATCH INSTRUCTIONS //////////
latch MIPS_latch_Inst(
    .clk(clk),
    .rst(rst),
    .en(IRWrite_w),

```

```

        .in(Inst_w),
        .out(InstLatched_w)
);
////////// LATCH DATA //////////
latch MIPS_latch_Data(
    .clk(clk),
    .rst(rst),
    .en(1'b1),
    .in(DataM_w),
    .out(DataMLatched_w)
);
////////// LATCH RD1 //////////
latch MIPS_latch_RD1(
    .clk(clk),
    .rst(rst),
    .en(1'b1),
    .in(Reg1_w),
    .out(Reg1Latched_w)
);
////////// LATCH RD2 //////////
latch MIPS_latch_RD2(
    .clk(clk),
    .rst(rst),
    .en(1'b1),
    .in(Reg2_w),
    .out(Reg2Latched_w)
);
////////// LATCH ALU //////////
latch MIPS_latch_ALU(
    .clk(clk),
    .rst(rst),
    .en(1'b1),
    .in(ALUResult_w),
    .out(ALUOut_w)
);

endmodule

```

Test Bench

```
`timescale 1ns/1ns
module MIPS_multicycle_tb;
reg clk_tb, rst_tb;
integer i;
MIPS_multicycle UUT (.clk(clk_tb), .rst(rst_tb));

initial begin
    clk_tb = 0; //initialize clock
    rst_tb = 1; //activate reset
    #2;
    rst_tb = 0; //deactivate reset
    #1080;
    for (i=0; i < 32; i=i+1) begin

$display("-----
-----");

        $display("PC=%d  ::  REG  MEMORY=>%d  ::  DATA  MEMORY=>%d", i,
UUT.MIPS_register_file.reg_mem[i], UUT.MIPS_data_memory.mem[i]);
    end
        $finish();
end
always forever #1 clk_tb = ~clk_tb;

initial begin
    $dumpvars(3, MIPS_multicycle_tb);
    $dumpfile("dump.vcd");
end
endmodule
```

CONTROL UNIT

```
`include "ALUControl.v"

`include "control_fsm.v"

module control_unit(

    input clk, rst,

    input [5:0] Opcode, Funct,

    /*-----Multiplexer Selects-----*/

    output MemtoReg, RegDst, ALUSrcA,

    output [1:0] ALUSrcB, PCSrc,

    /*-----Register enables-----*/

    output IRWrite, MemWrite, PCWrite, BEQ, BNE, RegWrite,

    /*-----ALU control-----*/

    output [3:0] ALU_Ctl

);

wire [1:0] ALUOp;

////////// CONTROL FSM //////////

control_fsm MIPS_control_fsm (

    .clk(clk),

    .rst(rst),

    .Opcode(Opcode),

    .MemtoReg(MemtoReg),

    .RegDst(RegDst),

    .ALUSrcA(ALUSrcA),

    .ALUSrcB(ALUSrcB),

    .PCSrc(PCSrc),
```

```

        .IRWrite(IRWrite),

        .MemWrite(MemWrite),

        .PCWrite(PCWrite),

        .BEQ(BEQ),

        .BNE(BNE),

        .RegWrite(RegWrite),

        .ALUOp(ALUOp)
    );

    //////////// ALU DECODER ////////////

    ALUControl MIPS_ALUControl (

        .ALUOp(ALUOp),

        .func_code(Funct),

        .ALU_Ctl1(ALU_Ctl1)
    );

endmodule

```

CONTROL FSM

```

module control_fsm (

    /*-----Input Variables-----*/

    input      clk, rst,

    input [5:0] Opcode,

    /*-----Multiplexer Selects-----*/

```

```

output reg      MemtoReg, RegDst, ALUSrcA,

output reg  [1:0] ALUSrcB, PCSrc,

/*-----Register enables-----*/

output reg  IRWrite, MemWrite, PCWrite, BEQ, BNE, RegWrite,

/*-----ALU control-----*/

output reg  [1:0] ALUOp);
reg [3:0] state;
reg [3:0] next_state;

// 1. CODIFICATION

//States

parameter Fetch      = 4'd0;
parameter Decode     = 4'd1;
parameter MemAdr     = 4'd2;
parameter Mem_Read   = 4'd3;
parameter Mem_Writeback = 4'd4;
parameter Mem_Write  = 4'd5;
parameter Execute    = 4'd6;
parameter ALU_Writeback = 4'd7;
parameter Branch_BEQ = 4'd8;
parameter Branch_BNE = 4'd9;
parameter Jump       = 4'd10;

//Opcodes

parameter Op_R      = 6'd0;

```

```

parameter Op_LW          = 6'd35;
parameter Op_SW          = 6'd43;
parameter Op_BEQ         = 6'd4;
parameter Op_BNE         = 6'd5;
parameter Op_Jump        = 6'd2;

```

```
// 2. STATE REGISTER
```

```
always @(posedge clk)
```

```
begin
```

```
    if ( rst )
```

```
        state <= Fetch;
```

```
    else
```

```
        state <= next_state;
```

```
end
```

```
// 3. NEXT STATE PROCESS
```

```
always @(state, Opcode)
```

```
begin
```

```
    case(state)
```

```
////////// STATES FOR EACH OPTION FROM THE INPUT //////////
```

```
// RESET MAIN VALUES
```

```
Fetch : next_state = Decode;
```

```
// INPUT STATE
```

```
Decode : begin
```



```

    if ( Opcode == Op_LW | Opcode == Op_SW ) // lw sw

        next_state = MemAdr;

    else if ( Opcode == Op_R ) // TYPE - R

        next_state = Execute;

    else if ( Opcode == Op_BEQ ) // BEQ

        next_state = Branch_BEQ;

    else if ( Opcode == Op_BNE ) // BNE

        next_state = Branch_BNE;

    else if ( Opcode == Op_Jump ) // JUMP

        next_state = Jump;

    else

        next_state = Fetch;
end

// SW OR LW STATE
MemAdr : begin

    if ( Opcode == Op_LW )

        next_state = Mem_Read;

    else if ( Opcode == Op_SW )

```

```

        next_state = Mem_Write;

    else        next_state = Fetch;
end

// LW READ STATE
Mem_Read : next_state = Mem_Writeback;

// LW FINAL STATE
Mem_Writeback : next_state = Fetch;

// SW STATE
Mem_Write : next_state = Fetch;

// R - TYPE STATE
Execute : next_state = ALU_Writeback;

// ALU WRITEBACK STATE
ALU_Writeback : next_state = Fetch;

// BRANCH IF EQUAL STATE
Branch_BEQ : next_state = Fetch;

// BRANCH IF NOT EQUAL STATE
Branch_BNE : next_state = Fetch;

// JUMP STATE
Jump : next_state = Fetch;

default : next_state = Fetch;
endcase

```

```

end

// 4. OUTPUT LOGIC PROCESS

always @(state)

    case (state)

        Decode : begin

            PCSrc      = 2'b00;

            ALUOp       = 2'b00;

            ALUSrcB     = 2'b10;

            ALUSrcA     = 1'b0;

            IRWrite     = 1'b0;

            MemWrite    = 1'b0;

            PCWrite     = 1'b0;

            BEQ         = 1'b0;

            BNE         = 1'b0;

            RegWrite    = 1'b0;

            MemtoReg    = 1'b0;

            RegDst      = 1'b0;

        end

        MemAdr : begin

            PCSrc      = 2'b00;

            ALUOp       = 2'b00;

            ALUSrcB     = 2'b10;

            ALUSrcA     = 1'b1;

```

```

        IRWrite      = 1'b0;

        MemWrite     = 1'b0;

        PCWrite      = 1'b0;

        BEQ          = 1'b0;

        BNE          = 1'b0;

        RegWrite     = 1'b0;

        MemtoReg     = 1'b0;

        RegDst       = 1'b0;

    end

    Mem_Read : begin

        PCSrc        = 2'b00;

        ALUOp        = 2'b00;

        ALUSrcB      = 2'b00;

        ALUSrcA      = 1'b0;

        IRWrite      = 1'b0;

        MemWrite     = 1'b0;

        PCWrite      = 1'b0;

        BEQ          = 1'b0;

        BNE          = 1'b0;

        RegWrite     = 1'b0;

        MemtoReg     = 1'b0;

        RegDst       = 1'b0;

    end

    Mem_Writeback : begin

```

```

        PCSrc      = 2'b00;

        ALUOp       = 2'b00;

        ALUSrcB     = 2'b00;

        ALUSrcA     = 1'b0;

        IRWrite     = 1'b0;

        MemWrite    = 1'b0;

        PCWrite     = 1'b0;

        BEQ         = 1'b0;

        BNE         = 1'b0;

        RegWrite    = 1'b1;

        MemtoReg    = 1'b1;

        RegDst      = 1'b0;

    end

    Mem_Write : begin

        PCSrc      = 2'b00;

        ALUOp       = 2'b00;

        ALUSrcB     = 2'b00;

        ALUSrcA     = 1'b0;

        IRWrite     = 1'b0;

        MemWrite    = 1'b1;

        PCWrite     = 1'b0;

        BEQ         = 1'b0;

        BNE         = 1'b0;

        RegWrite    = 1'b0;

```

```

        MemtoReg    = 1'b0;

        RegDst      = 1'b0;

    end

    Execute : begin

        PCSrc        = 2'b00;

        ALUOp         = 2'b10;

        ALUSrcB       = 2'b00;

        ALUSrcA       = 1'b1;

        IRWrite       = 1'b0;

        MemWrite      = 1'b0;

        PCWrite       = 1'b0;

        BEQ            = 1'b0;

        BNE            = 1'b0;

        RegWrite      = 1'b0;

        MemtoReg      = 1'b0;

        RegDst        = 1'b0;

    end

    ALU_Writeback : begin

        PCSrc         = 2'b00;

        ALUOp          = 2'b00;

        ALUSrcB        = 2'b00;

        ALUSrcA        = 1'b0;

        IRWrite        = 1'b0;

```

```

        MemWrite    = 1'b0;

        PCWrite     = 1'b0;

        BEQ         = 1'b0;

        BNE         = 1'b0;

        RegWrite    = 1'b1;

        MemtoReg    = 1'b0;

        RegDst      = 1'b1;

    end

    Branch_BEQ : begin

        PCSrc       = 2'b01;

        ALUOp       = 2'b01;

        ALUSrcB     = 2'b00;

        ALUSrcA     = 1'b1;

        IRWrite     = 1'b0;

        MemWrite    = 1'b0;

        PCWrite     = 1'b0;

        BEQ         = 1'b1;

        BNE         = 1'b0;

        RegWrite    = 1'b0;

        MemtoReg    = 1'b0;

        RegDst      = 1'b0;

    end

    Branch_BNE : begin

        PCSrc       = 2'b01;

```

```

        ALUOp      = 2'b01;

        ALUSrcB    = 2'b00;

        ALUSrcA    = 1'b1;

        IRWrite    = 1'b0;

        MemWrite   = 1'b0;

        PCWrite    = 1'b0;

        BEQ        = 1'b0;

        BNE        = 1'b1;

        RegWrite   = 1'b0;

        MemtoReg   = 1'b0;

        RegDst     = 1'b0;

end

Jump : begin

        PCSrc      = 2'b10;

        ALUOp      = 2'b00;

        ALUSrcB    = 2'b00;

        ALUSrcA    = 1'b0;

        IRWrite    = 1'b0;

        MemWrite   = 1'b0;

        PCWrite    = 1'b1;

        BEQ        = 1'b0;

        BNE        = 1'b0;

        RegWrite   = 1'b0;

        MemtoReg   = 1'b0;

```



```

        RegDst      = 1'b0;

    end

    default : begin//Fetch

        PCSrc      = 2'b00;

        ALUOp       = 2'b00;

        ALUSrcB     = 2'b01;

        ALUSrcA     = 1'b0;

        IRWrite     = 1'b1;

        MemWrite    = 1'b0;

        PCWrite     = 1'b1;

        BEQ         = 1'b0;

        BNE         = 1'b0;

        RegWrite    = 1'b0;

        MemtoReg    = 1'b0;

        RegDst      = 1'b0;

    end

endcase

endmodule

```

ALU

```
module ALU (  
  
    input [3:0] ALU_Ctl, //from ALU //book 317  
  
    input [31:0] A,B,  
  
    output reg [31:0] ALUOut,  
  
    output Zero);  
  
    assign Zero = (ALUOut == 0);  
  
    always @(ALU_Ctl, A, B) begin  
  
        case (ALU_Ctl)  
  
            0: ALUOut = A & B;  
  
            1: ALUOut = A | B;  
  
            2: ALUOut = A + B;  
  
            6: ALUOut = A - B;  
  
            12:ALUOut = A < B ? 1:0;  
  
            default: ALUOut = 0;  
  
        endcase  
  
    end  
  
endmodule
```

ALU CONTROL

```
module ALUControl (  
  
    input [1:0] ALUOp, //from CU  
  
    input [5:0] func_code, // 5:0  
  
    output reg [3:0] ALU_Ctl // to ALU  
  
);
```

```

always @(ALUOp, func_code) begin

    if (ALUOp == 0)

        ALU_Ctl = 2;    //LW and SW use add

    else if (ALUOp == 1)

        ALU_Ctl = 6;    // branch if equal

    else

        case (func_code)

            //pag. 317

            32: ALU_Ctl = 2; //add

            34: ALU_Ctl = 6; //subtract

            36: ALU_Ctl = 0; //AND

            37: ALU_Ctl = 1; //OR

            42: ALU_Ctl = 12; //slt

            default: ALU_Ctl = 4'hf;

        endcase

    end

endmodule

```

DATA MEMORY

```

module data_memory (

    input clk,

    input [31:0] address,

```

```

    input memWrite,

    input [31:0] writeData,

    output [31:0] readData

);

reg [31:0] mem[0:255]; //32 bits memory with 256 entries

initial begin

    $readmemb("data_mem.txt", mem); /**ESCRITURA

end

always @ (posedge clk) begin

    if (memWrite) begin

        mem[address] = writeData;

        $writememb("data_mem.txt", mem);

    end

end

assign readData = mem[address];

endmodule

```

INSTRUCTIONS MEMORY

```

module inst_mem(

    input [31:0] address,

    output [31:0] inst);

reg [31:0] Mem [0:255];

```

```

    initial begin

        $readmemb("instructions.txt", Mem);

    end

    assign inst = Mem[address];

endmodule

```

FILE REGISTER

```

module register_file(

    input clk,

    input regWrite,

    input [4:0] readReg1, readReg2, writeReg,

    input [31:0] writeData,

    output [31:0] readData1, readData2);

    reg [31:0] reg_mem [31:0]; //32 registers of 32 bits

    /*----- Initialize all registers in 0-----*/

    initial begin

        $readmemb("regMem.txt", reg_mem);

    end

    /*----- Save one register -----*/

    always @ (posedge clk) begin

        if(regWrite) begin

            reg_mem[writeReg] = writeData;


```

```

        $writememb("regMem.txt", reg_mem);

    end

end

/*----- Read the 2 registers-----*/

    assign readData1 = reg_mem[readReg1];

    assign readData2 = reg_mem[readReg2];

endmodule

```

SIGN EXTENDER

```

module SignExt (

    input [15:0] data_in,

    output [31:0] data_out

);

    assign data_out = {{16{data_in[15]}},data_in};

endmodule

```

MULTIPLEXER

```

module mux2to1

#(parameter WORD_LENGTH = 32)

(input sel,

    input [WORD_LENGTH-1 : 0] Data_0, Data_1,

    // Output Ports

    output [WORD_LENGTH-1 : 0] Mux_Output);

    assign Mux_Output = (sel) ? Data_1: Data_0;

endmodule

```

```

module mux3to1

#(parameter WORD_LENGTH = 32)

(

    input [1:0] sel,

    input [WORD_LENGTH-1 : 0] Data_0, Data_1, Data_2,

    output reg [WORD_LENGTH-1 : 0] Mux_Output);

always @(*) begin

    case (sel)

        0: Mux_Output = Data_0;

        1: Mux_Output = Data_1;

        2: Mux_Output = Data_2;

        default: Mux_Output = 0;

    endcase

end

endmodule

```

BRANCH DECODER

```

module branch_decoder(

    input beq, bne, pcwrite, zero,

    output ctrl);

    assign ctrl = (bne&~zero) | (beq&zero) | (pcwrite);

endmodule

```

LATCH

```
module latch(clk, rst, en, in, out);  
  
    input clk, rst, en;  
  
    input [31:0] in;  
  
    output reg [31:0] out;  
  
    always @(posedge clk) begin  
  
        if (rst)  
  
            out <= 0;  
  
        else if (en)  
  
            out <= in;  
  
    end  
  
endmodule
```

 

DETAILED DESCRIPTION OF VERIFICATION PROCESS

TEST PROGRAM

Given five numbers, the test program orders them from greatest to least. For example, given the numbers 1, 66, 117, 88, 19, the output of the algorithm orders them in the form 117, 88, 66, 19, 1.

OBJECTIVE

The algorithm implemented is known as “Bubble sort” that consists of comparing each value with the rest and making the changes if the condition “<” between the two numbers is true. The graphical process of this algorithm is shown below.




DESIRED RESULTS

On Data Memory, program would show the next information:

Data Segment					
Address	Value (+0)	Value (+4)	Value (+8)	Value (+c)	Value (+10)
0x10010000	0x00000075	0x00000058	0x00000042	0x00000013	0x00000001

PROGRAM FLOWCHART

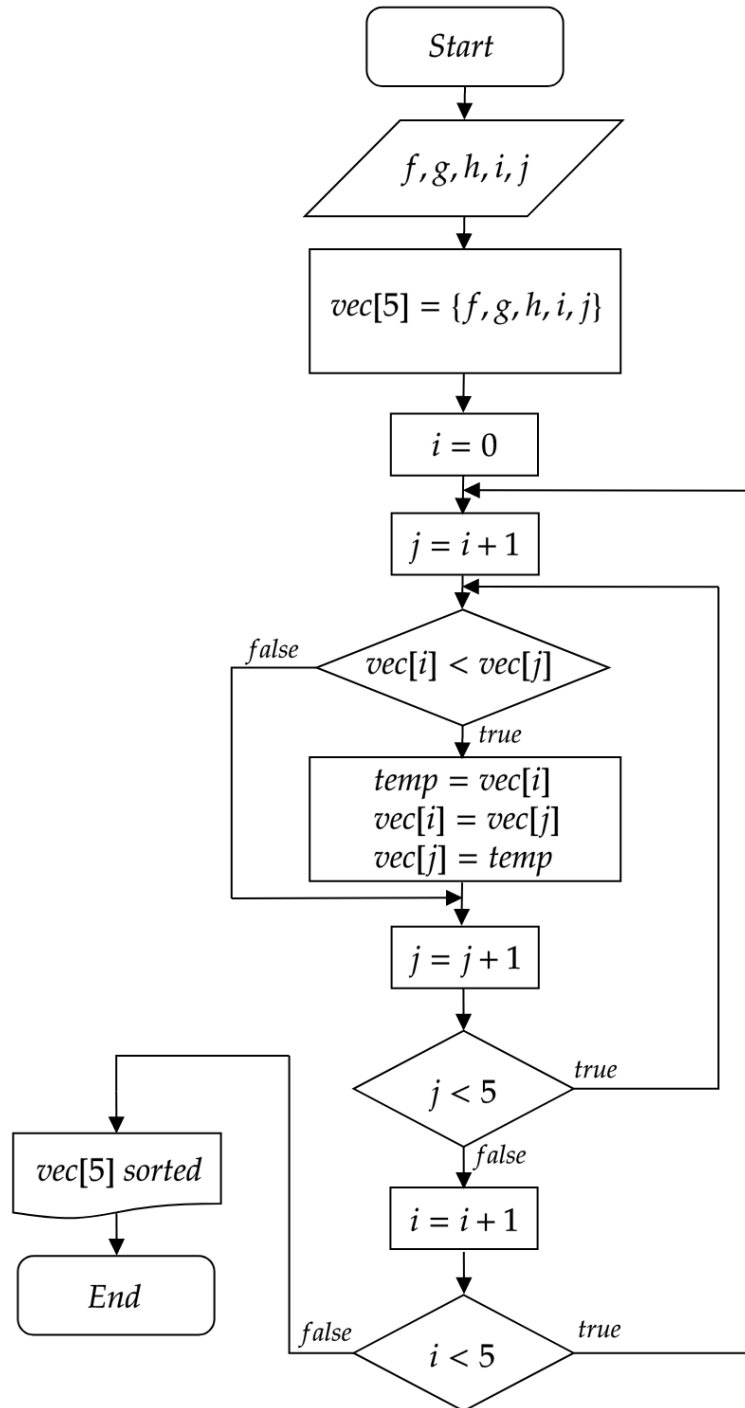The flow chart for the code implemented to sort the numbers (as described above) is the following:



C CODE

With the flow chart elaborated, the next step is to write a code in C language that works as intended. The result is shown below.

```
#include <stdio.h>
#include <stdlib.h>

int main ()
{

    int vec [5] = {0}; //Array used to store values
    int i=0, j=0; //Control variables used in For loops
    int temp; //Integer used to save previous values of vec[i]
                //to change places with vec[j]

    //Data request from monitor, to be saved in vec array
    for(i=0; i<5; i++){
        printf("Ingresa numero %d:", i+1);
        scanf("%d", &vec[i]);
    }

    // Sorting algorithm, order the values from greatest to lowest
    for(i=0; i<5; i++){
        for(j=i+1; j<5; j++){
            if(vec[i]<vec[j]){
                temp=vec[i]; //Save current value of vec[i]
                vec[i]=vec[j]; //Replace value of vec[i] with vec[j]
                vec[j]=temp; //Save previous value of vec[i] into vec[j]
            }
        }
    }


    putchar('\n'); // jump one line to display correctly
    for(i=0; i<5; i++){
        printf(" %d\n", vec[i]); //Display sorted values
    }

    return 0;
}
```

ASSEMBLER AND MACHINE CODE

labels	Assembly instruction	Type	Binary machine code
	lw \$s1,5(\$0)	I	10001100000100000000000000000000
	lw \$t8,6(\$0)	I	10001100000110000000000000000000
	lw \$t5,7(\$0)	I	10001100000011000000000000000000
	lw \$s0,8(\$0)	I	10001100000100000000000000000000
FOR_i:	beq \$t8, \$s1, DONE_i	I	00010011000100010000000000000000
	add \$t9, \$t8,\$t5	R	00000011000011011100100000000000
FOR_j:	beq \$t9, \$s1, DONE_j	I	00010011001100010000000000000000
	add \$t0, \$t8, \$s0	R	00000011000100000100000000000000
	lw \$t1, 0(\$t0)	I	10001101000010000000000000000000
	add \$t2, \$t9, \$s0	R	00000011001100000101000000000000
	lw \$t3, 0(\$t2)	I	10001101010010100000000000000000
	slt \$t4, \$t1, \$t3	R	00000001001010110110000000000000
IF:	beq \$t4,\$0, EXIT_IF	I	00010001100000000000000000000000
	lw \$t7,0(\$t0)	I	10001101000011100000000000000000
	sw \$t3,0(\$t0)	I	10101101000010100000000000000000
	sw \$t7,0(\$t2)	I	10101101010011100000000000000000
EXIT_IF:	add \$t9,\$t9,\$t5	R	00100011001110010000000000000000
	j FOR_j	J	00001000000100000000000000000000
DONE_j:	add \$t8, \$t8, \$t5	R	00100011000110000000000000000000
	j FOR_i	J	00001000000100000000000000000000
DONE_i:			

RESULTS

 

```
# Time: 0 ps Iteration: 0 Process: /MIPS_multicycle_tb/#INITIAL#35 File: C:/quartus/Diplomado/mips_multi_cycle/MIPS_multicycle_tb.v Line: 37
# -----
# PC=      0 :: REG MEMORY=>      0 :: DATA MEMORY=>      117
# -----
# PC=      1 :: REG MEMORY=>      0 :: DATA MEMORY=>      88
# -----
# PC=      2 :: REG MEMORY=>      0 :: DATA MEMORY=>      66
# -----
# PC=      3 :: REG MEMORY=>      0 :: DATA MEMORY=>      19
# -----
# PC=      4 :: REG MEMORY=>      0 :: DATA MEMORY=>      1
```

EDA Playground PROJECT LINK

The link for the Project on EDA Playground is:

<https://www.edaplayground.com/x/m3EN>

CONCLUSIONS

Making a multicycle Mips processor required a lot of work on every detail and running test by test in order to improve the main code without errors, so it was developed module by module and when each of them was able to work properly, add it to the top program.

On the other hand, there was some issues while creating the program as each module have a different purpose and even if they worked in the testing alone, at the time it was added to the program, some problems were discovered an step by step solved by looking for the malfunctioning area and adapting it to the goal of the processor.

Creating a processor in this way is an excellent opportunity to understand and even improve the functionality of it by researching and analyzing each part that composes the structure. This project leaves the team the knowledge needed to be aware of the processes that involve a processor and let us modify it to an improved framework with less coding and/or better understandability when reviewing the program.

FUTURE WORK

After the implementation of this microprocessor in its multicycle configuration, it is planned to develop verification tests using Systemverilog/UVM as part of the course.

REFERENCES

- Hennessy, J. and Patterson, D., n.d. *Computer architecture*. 6th ed.
- https://link.springer.com/chapter/10.1007/978-3-642-68402-9_37
- <https://resources.pcb.cadence.com/blog/2020-hardware-description-languages-vhdl-vs-verilog-and-their-functional-uses>
- <https://www.dsi.uclm.es/personal/FcoAlfaro/pfc/TFG%20Pablo%20Abril.pdf>